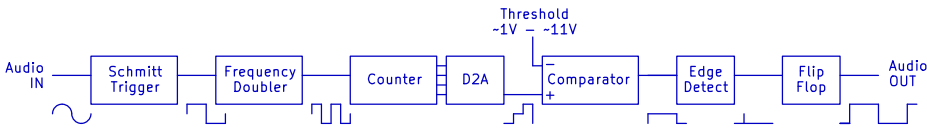


Subharmolizer

Eurorack Module to generate a square wave subharmonic of an input audio signal

Block Diagram



Issues with rev1

- 1. needs frontend filter to remove freqs > ~4kHz
(or: the frequency doubler needs tweaking to support higher freqs)
- 2. output vol seems v low
- 3. need to add CV override to Threshold input
- 4. phase of output is unpredictable – freq doubler can see a –ve change before a +ve one
- 5. bonkersness when Threshold set very close to an exact level coming from D2A
maybe need some hysteresis?
- 6. might be nice to add a second counter to allow for more subharms
or perhaps use a CD4024 or such instead of CD4516 – we’re not using the preset
- 7. output square wave has a significant spike on the leading edge

Schematic




File: subharmolizer–schem.kicad_sch

molen, inc.

Sheet: /
File: subharmolizer–rev2.kicad_sch

Title: Subharmolizer Overview

Size: A4	Date: 2025–09–20	Rev: 2
KiCad E.D.A. 9.0.4		Id: 1/2

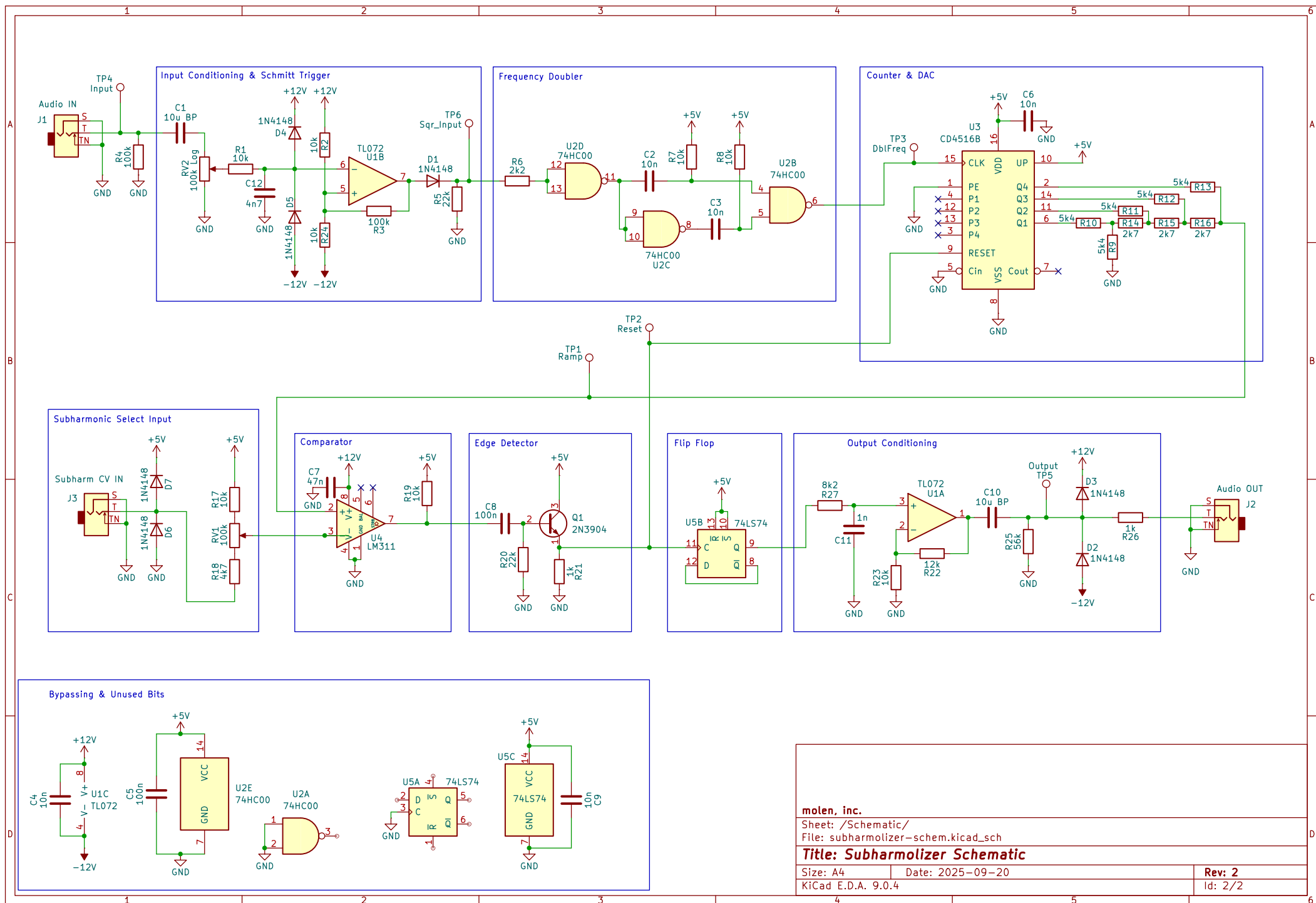

molen, inc.

Sheet: /Schematic/
File: subharmonizer-schem.kicad_sch

Title: Subharmonizer Schematic

Size: A4 Date: 2025-09-20

KiCad E.D.A. 9.0.4

Rev: 2

Id: 2/2